

Lecture 5

Parts/design Choices

(Part 1)

IR Sensor

- Consists of IR LED(transmitter/emitter) and IR receiver(transistor type most likely)
- Wavelengths much match between emitter and receiver
- Pulsing high current to raise Signal/Noise ratio
- Use voltage divider for receiver converting current signal to voltage signal


Specs for IR Emitter

- Specs need to know when choosing an IR Emitter:
 1. Wavelength
 2. Voltage drop
 3. DC Forward current
 4. Pulsing current/timing
 5. Viewing angle(full angle)
 6. Radiant Intensity

Wavelength

- 950nm and 850nm are the 2 most popular choices for IR emitter
- You need to find IR receive that matches the wavelength of emitter in order to max power efficiency

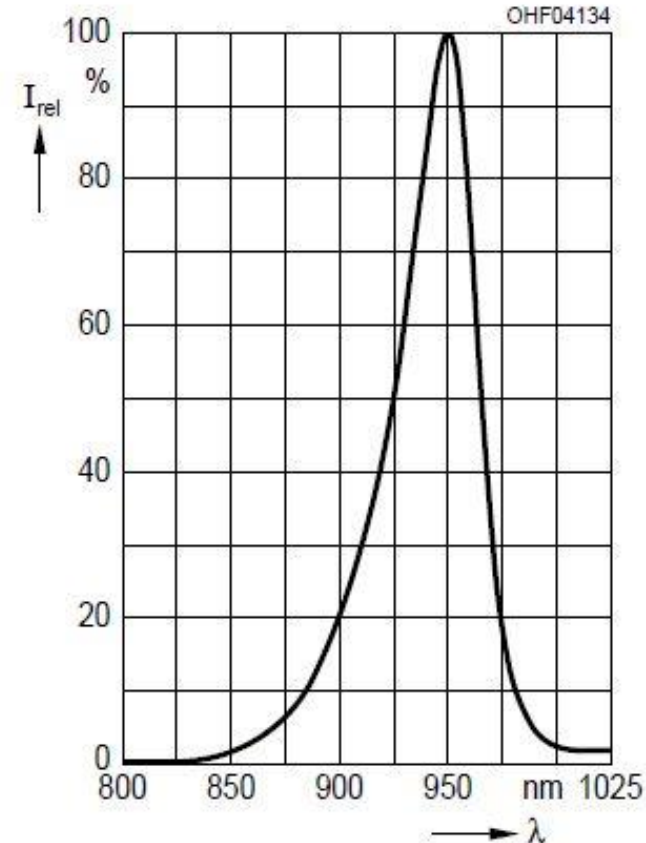
Relative Spectral Emission
 $I_{\text{rel}} = f(\lambda)$



Voltage Drop

- IR Emitter is essentially an LED that emits infrared
- And LED is essentially a diode, and diode drops voltage
- Voltage drop varies depends of the expected current
- Examples:
 - SFH4550 drops 1.5V @100mah
 - SFH4545 drops 1.5V @100mah
 - SFH4511 drops 1.3V @ 100mah(discontinued)

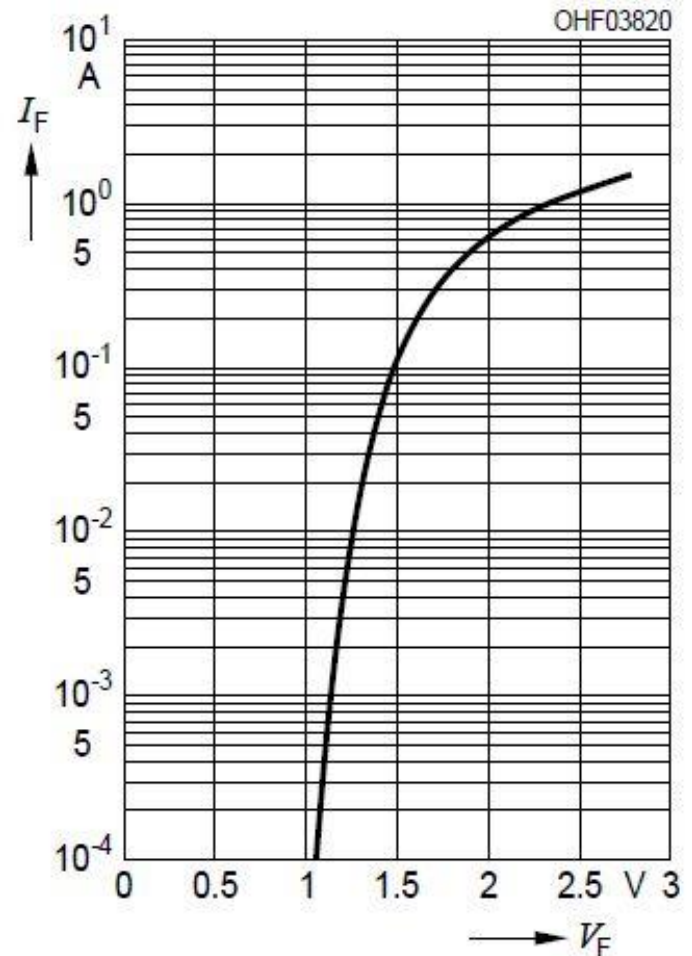Forward Current $I_F = f(V_F)$
Single pulse, $t_p = 100 \mu\text{s}$




DC Forward Current

- Means the max constant current that the IR emitter can safely handle(max limit)
- Usually 100mah for typical 5mm diameter IR LED, 50mah for 3mm diameter IR LED. Some metal shield package version has even higher DC forward current
- DC forward current somehow indicates the capability of IR Emitter when pulsing at high current

Pulsing Current

- LED allows pulsing current higher than DC forward current during a short time period
- Max Capability are different at different turn on time
- Exceeding max cap will damage the IR LED
- Should always check table to ensure your time/current choice for your design


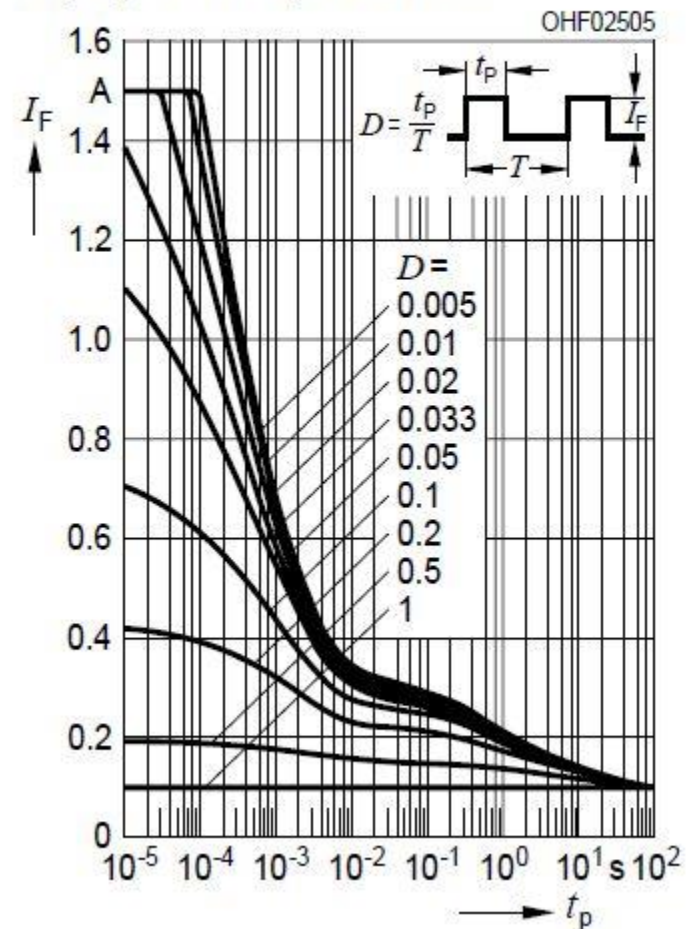
Permissible Pulse Handling Capability $I_F = f(\tau)$, $T_A = 25^\circ\text{C}$,
duty cycle $D =$ parameter



Viewing angle

- Smaller angle is preferred for higher power intensity and more accurate distance detect, usually under 10 degree

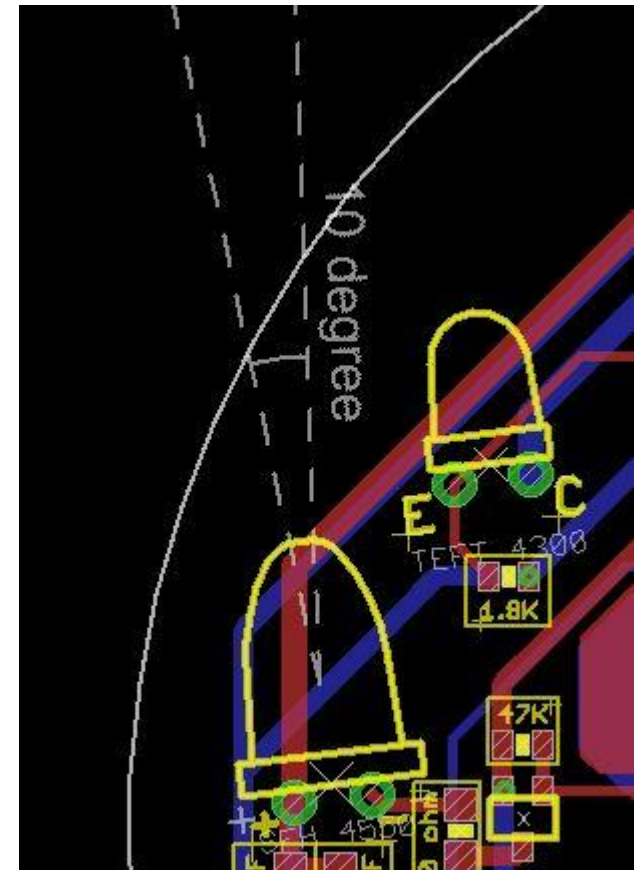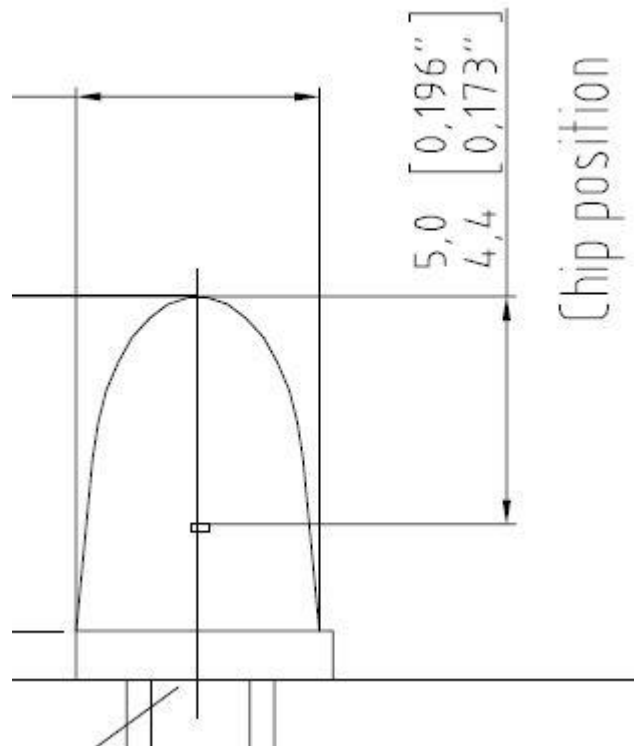Chip position indicates where the IR light starts to emit



Radiant Intensity

- Indicates the power intensity per unit area
- Varies between different models
- The higher the better
- 850nm type has higher Intensity than 950nm in general
- Example:
 - SFH4550(850nm)6^{degree} 630mW/sr @ 100mA
 - SFH4545(950nm)10^{degree} 550mW/sr @ 100mA
 - SFH4511(940nm)8^{degree} 63mW/sr @
100mA(discontinued)

Some other important facts

- Package:
 - T 1 $\frac{3}{4}$ is about 5mm diameter package
 - T1 is about 3mm diameter package
- Through hole preferred for the availability and efforts on mounting it on the mouse
- Choices are pretty obvious when you use the filter on vendor's site(ie. Mouser,digikey, etc) when you apply the preferred specs

IR Receiver


- Viewing angles are always wider than emitter
- Angles are between 30-60 degree
- Receiver has sensitive wavelength range, as long as it covers the wavelength for IR emitter
- The resistance of the resistor that serial with is based on your own test and preference.
Resistance value will affect the max reading value and receiver charge/discharge time
- Faster charging time saves pulsing time but could be too sensitive, slower charging time takes more time but less sensitive(less sensitive for ambient noise)

Matching wavelength

Emitter(SFH4545)

Relative Spectral Emission

$$I_{\text{rel}} = f(\lambda)$$

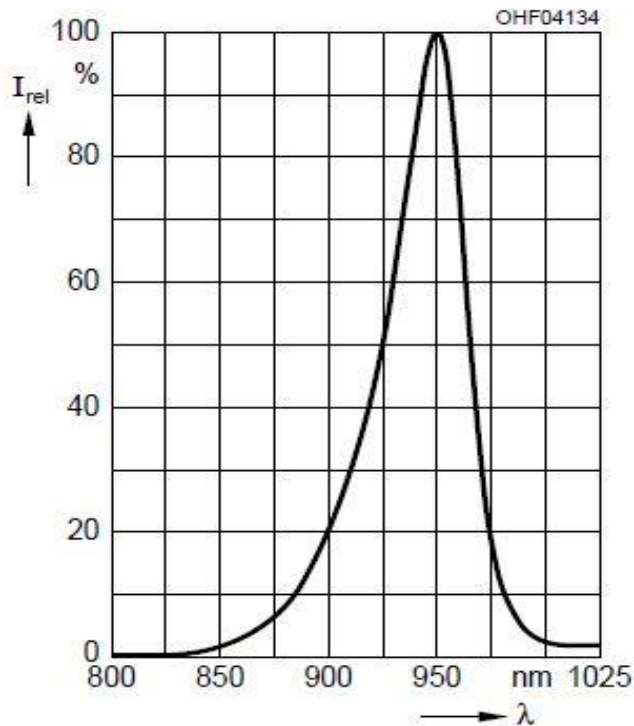

Receiver(TEFT4300)

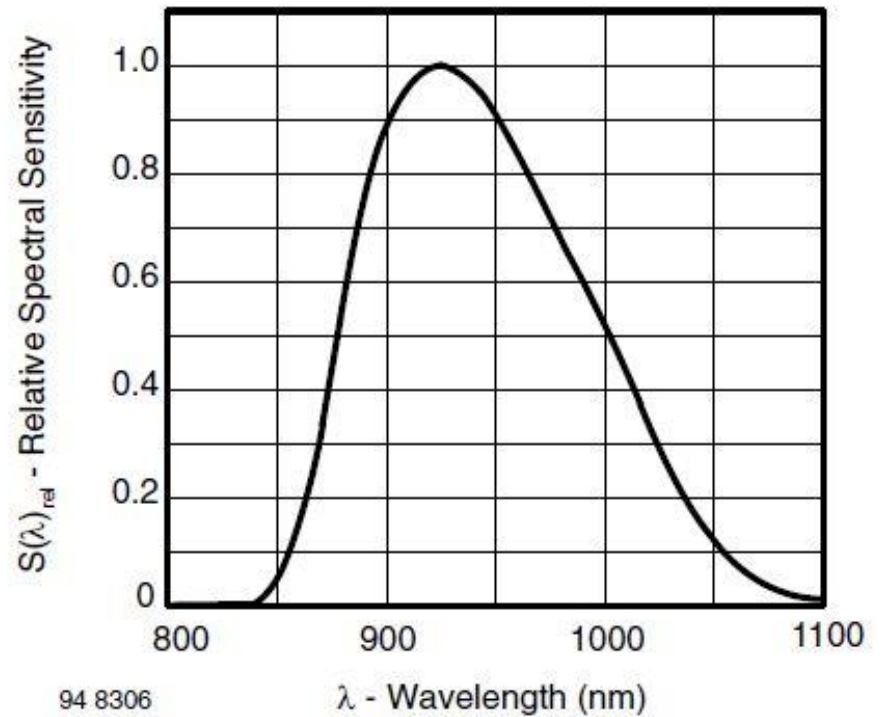


Fig. 7 - Relative Spectral Sensitivity vs. Wavelength

Receiver₊

Power Supply


- Use 2 lipo Batteries serial at 7.4V at V_{bat}
- Use 2mm pitch JST male plug mount on PCB
- 2.54mm or 2mm pitch slide switches are usually used, pay attention with power rating
- Large value tantalum capacitors are used to stabilized the power supply, pay attention of the max voltage and ESR(equivalent serial resistance) of tantalum capacitor

Power Supply(cont.)

- 3 different voltage usage in system
 - v_{bat} for motor driver and voltage meter
 - 5V for IR emitter and encoder power supply
 - 3.3V for rest of the sytem
- Current consumption level
 - Motor(V_{bat})>5V(emitter)>3.3V
- Choice on Futura Kit Mouse
 - 5V LVO regulator with 1A max output
 - 3.3V LVO regulator with 400mah max output
- Sufficient current with the regulator chosen above
- The voltage drop for LVO regulator is as low as possible(especially for 5V regulator)


Power Supply(digital)

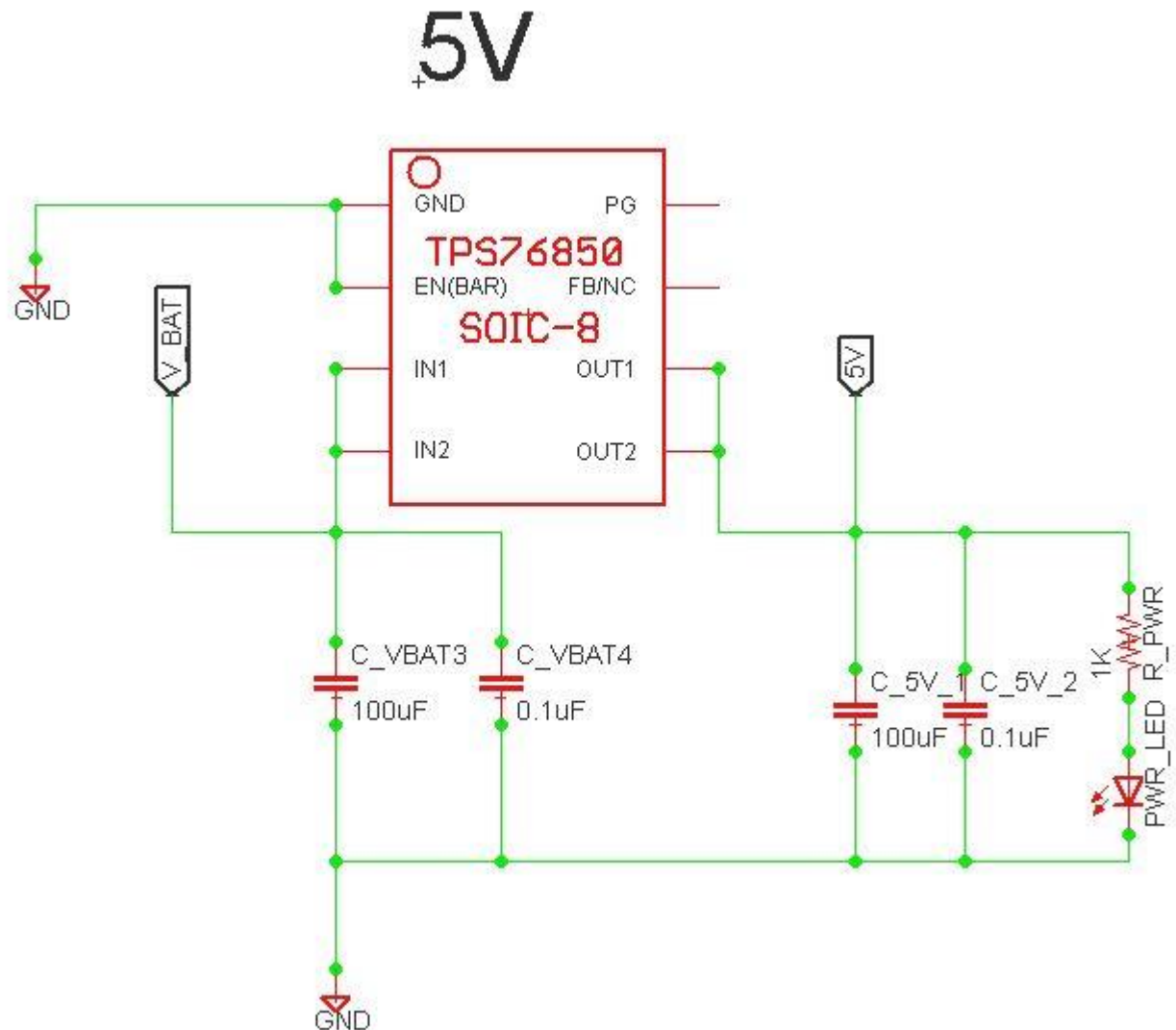- Add by pass cap before and after to stabilize supply
- Add low pass cap before and after to filter out high freq. noise





Power Supply(analog)

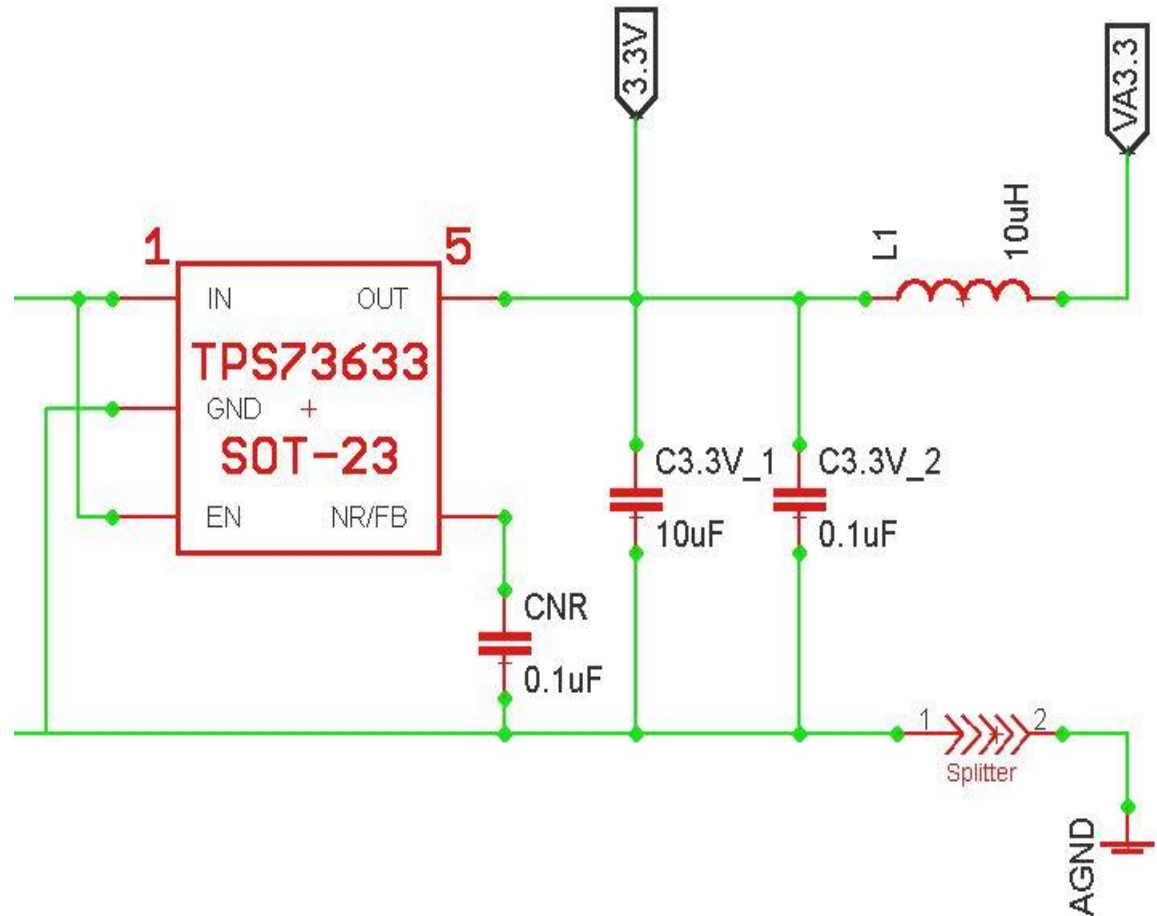- Separate ground is preferred to reduce the noise to analog device
- Usually serial a inductor between supply and analog supply to stabilized the analog power supply



Power Supply(motor)

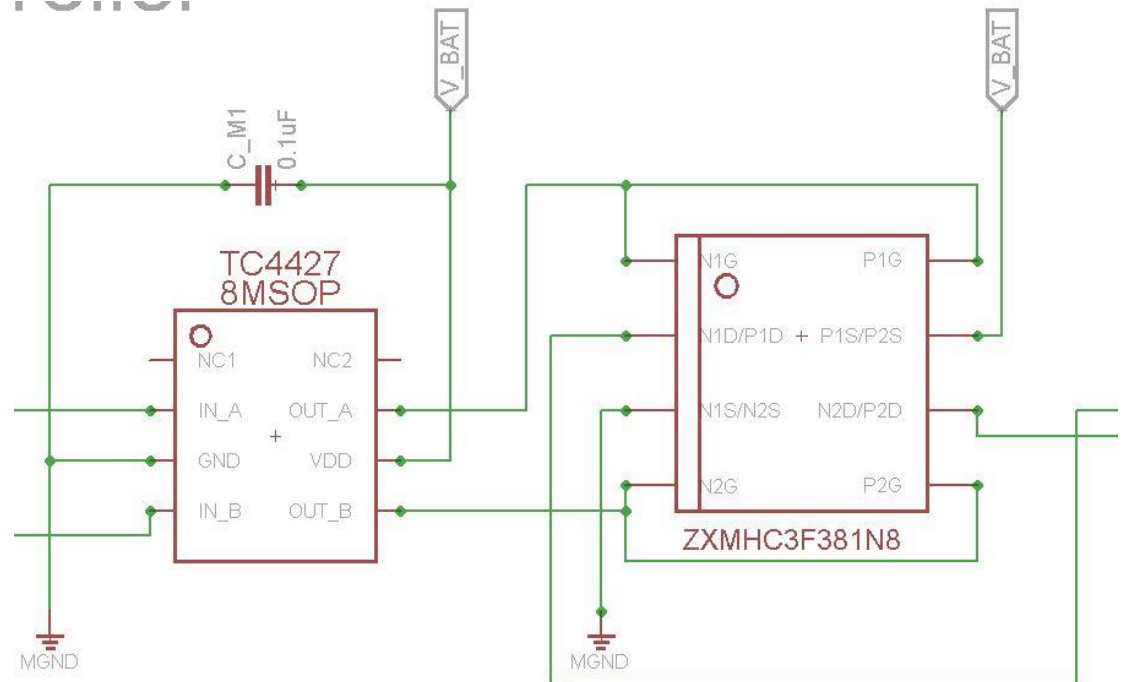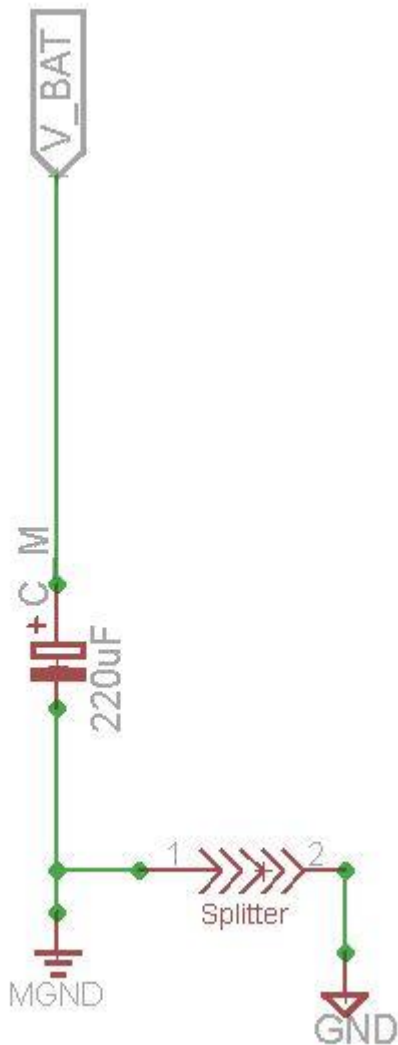- Tantalum cap to supply motor power(place very close to motor driver)
- Low pass filtering cap very close to motor driver
- Separate ground for motor



RCL selection

- Smaller package leaves you more space on mouse, harder to solder, and higher ESR
- Package on Futura Kit Mouse:
 - 0603 resistor for IR Emitter(250mw rating, because of high current)
 - 0402 resistor for rest of the system
 - 1220(in) tantalum cap for 100uF 2917(in) tantalum cap for 220uF(motor supply)
- 0603 caps for rest of the system
- 1007 10uF Inductor
- RCL availability in lab
 - 0402 resistor stocked for all value you need for micromouse
 - 0603 capacitor stocked for all value you need for micromouse

Pay attention of the max voltage of the cap and power rating for resistor